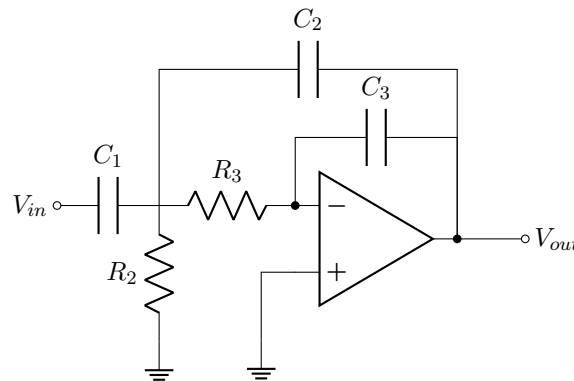


## Single channel


### Filter.

This is a second order MFB (Multiple feed back Band Pass Filter). By changing  $R_2$ ,  $C_1$ ,  $C_2$ ,  $C_3$  we can change the cut-off frequency.


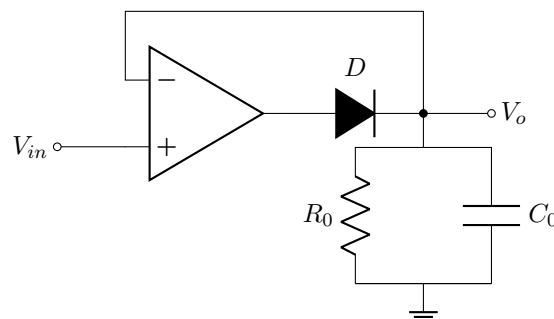
### Peak Detector.

We need to examine how the peaks change in each frequency component so that we can display them. For more reliable results we use Op Amp based peak detector rather than single diode peak detector.




### Comparator.

We need to map peak detector output to number of LEDs which is proportional to its amplitude. We could use Op amp comparators for this but for 10 bands which include  $10 \times 10 = 100$  we require 100 opamps which is not practical. Hence we use LM3914 IC which has 10 comparators.

This IC has two modes. Dot & Bar mode. Let's use bar mode for Visually appealing.

**From Datasheet;**

## TYPICAL APPLICATIONS

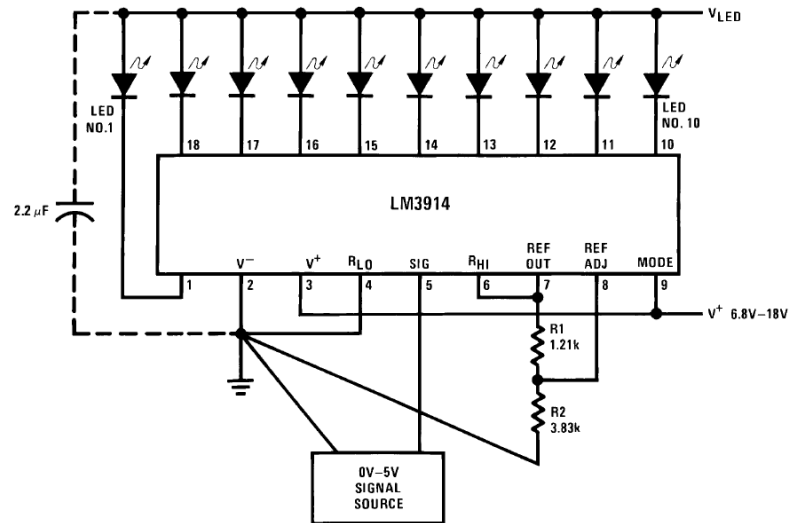

$$V_{Ref} = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$$

$$I_{LED} \cong \frac{12.5}{R_1}$$

$$V_{Ref} = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$$

$$I_{LED} \cong \frac{12.5}{R_1}$$

Since Audio source typical ( $V_{out}$ ) max  $\approx 2.5V$

Choose  $V_{Ref} = 2.5V = 1.25 \left( 1 + \frac{R_2}{R_1} \right)$


Hence  $R_1 = R_2$

Choose current per led to be 10 mA

$$I_{LED} = 10 \text{ mA} = \frac{12.5}{R_1}$$

$$\Rightarrow R_1 = 1.25 \text{ k}\Omega$$

**Combined Circuit per channel.**

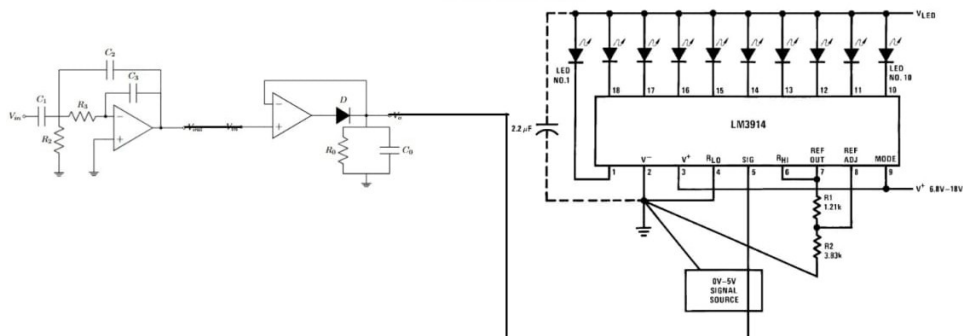

Repeat the above circuit to create 10 channels. Diagram of full circuit.